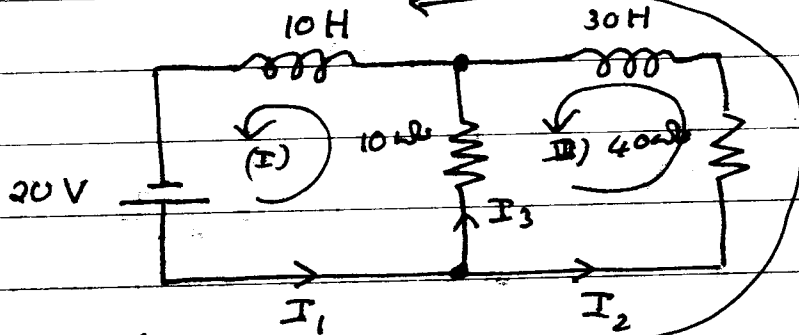


(4)

#10 Assume all initial currents are zero.



$$E_R = RI$$

$$(II) \quad E_L = L \frac{dI}{dt}$$

$$E_C = \frac{1}{C} \frac{dq}{dt}$$

By Kirchhoff's Voltage Law:

$$\text{Loop (I)}: 10 I_3 + 10 \frac{dI_1}{dt} = 20 \quad (a)$$

$$\text{Loop (II)}: 40 I_2 + 30 \frac{dI_2}{dt} + 10 I_3 = 20 \quad (b)$$

$$\text{Loop (III)}: 40 I_2 + 30 \frac{dI_2}{dt} - 10 I_3 = 0 \quad (c)$$

Note: Equation (c) follows from (b)-(a)

By Kirchhoff's current law:

$$I_1 = I_2 + I_3 \quad (d)$$

From (a) & (d)

$$10 I_3 + 10 (\dot{I}_2 + \dot{I}_3) = 20$$

$$\text{or } I_3 + \dot{I}_2 + \dot{I}_3 = 2$$

$$\text{From (c), } I_3 = 4 I_2 + 3 \dot{I}_2 \Rightarrow \dot{I}_2(0) = 0 \text{ since } I_3(0) = I_2(0) = 0.$$

$$\ddot{I}_3 = 4 \dot{I}_2 + 3 \ddot{I}_2$$

$$I_3 + \dot{I}_3 = 4 I_2 + 7 \dot{I}_2 + 3 \ddot{I}_2$$

$$I_3 + \dot{I}_3 + \dot{I}_2 = 4 I_2 + 8 \dot{I}_2 + 3 \ddot{I}_2$$

We solve

$$3 \ddot{I}_2 + 8 \dot{I}_2 + 4 I_2 = 2, \quad I_2(0) = \dot{I}_2(0) = 0.$$